

Experiment 6: Music

Raghav Singhal, 19D070049
EE-214, WEL, IIT Bombay
April 1, 2021

Overview of the experiment:

The purpose of the experiment was to design a circuit with the following specification: The circuit played notes in a particular sequence, as is done in music. The different notes were generated using the entity designed in the last experiment, while an FSM was used to automate the sequential order and duration of the notes. A switch is used as reset.

I first designed a logic circuit and drew a schematic to meet the specifications. This was followed by describing the logic circuit in behavioural VHDL, and simulating the circuit using the test-bench to confirm its correct functioning. The circuit was then mapped to the Krypton Board, interfaced with the speaker, and the music was played.

This report will outline the design ideology and results in the following order:

- Approach used to meet the specifications
- Design implementation in VHDL (including snaps of code of the main logic components)
- RTL simulation
- Mapping on the Krypton Board
- Observations

Approach to the experiment:

Notes Table:

NOTES TABLE:


Note	Pa	Pa	Dha	Pa	Ma	Ga	Ma	Ma	Pa	Ma	Ga	Re
Duration	0.5	0.5	0.25	0.25	0.25	0.25	0.5	0.5	0.25	0.25	0.25	0.25
Count	1,2	3,4	5	6	7	8	9,10	11,12	13	14	15	16

Note	Ga	Ga	Ma	Ga	Re	Sa	Ni	Re	Sa	Sa	Silent	Silent
Duration	0.5	0.5	0.25	0.25	0.25	0.25	0.5	0.5	0.25	0.25	0.25	0.25
Count	17,18	19,20	21	22	23	24	25,26	27,28	29	30	31	32

State Table:

STATE TABLE				
	Present State	Count	Next State	Output (to tone generator)
①	Sa	29	Sa	
		24	Ni	1000 0000
		30	Silent	
②	Re	23, 28	Sa	
		27	Re	0100 0000
		16	Ga	
③	Ga	15, 22	Re	
		17, 18, 19	Ga	0010 0000
		8, 20	Ma	
④	Ma	7, 14, 21	Ga	
		9, 10, 11	Ma	0001 0000
		12	Pa	
⑤	Pa	6, 13	Ma	
		1, 2, 3	Pa	0000 1000
		4	Dha	
⑥	Dha	5	Pa	0000 0100
⑦	Ni	26	Re	
		25	Ni	0000 0010
⑧	Silent	31	Silent	
		0, 32	Pa	0000 0001

State Transition Diagram:

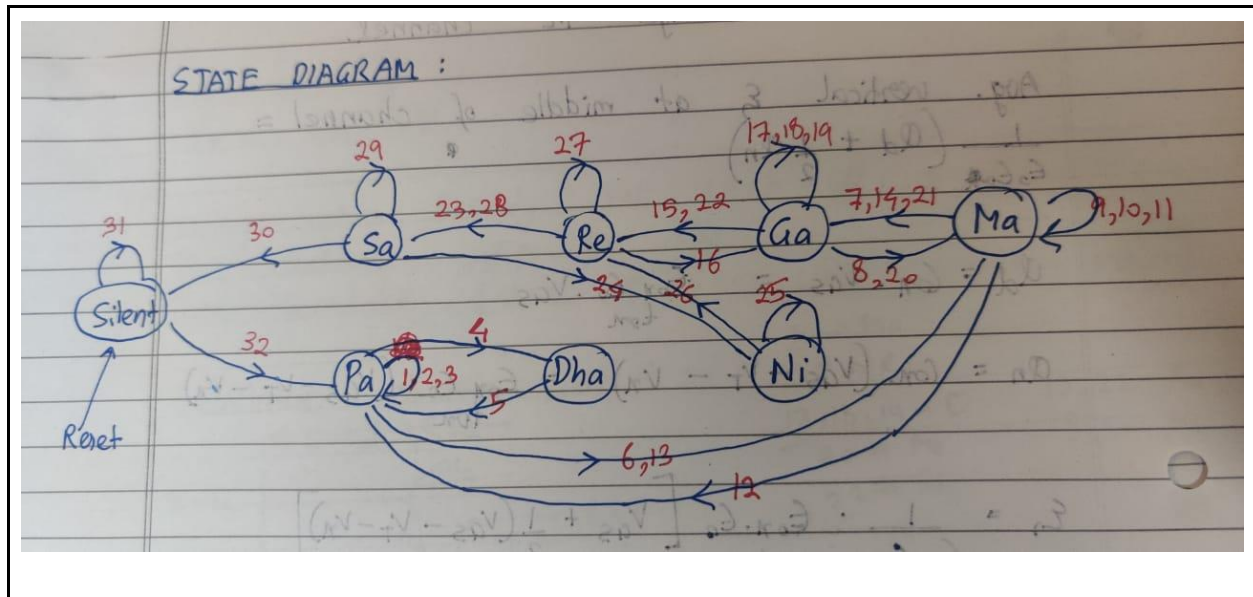

Design document and VHDL code if relevant:

VHDL code for music.vhdl:

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.ALL;
3
4  entity music is
5  port (toneOut : out std_logic;
6        clk_50, resetn : in std_logic;
7        LED : out std_logic_vector(7 downto 0));
8  end entity music;
9
10 architecture fsm of music is
11  -- Fill all the states
12  -----Code here-----
13  -- Declare state types here
14  type state_type is (sa, re, ga, ma, pa, dha, ni, silent);
15
16  -- Declare all necessary signals here
17  signal y_present : state_type := silent;
18  signal switch : std_logic_vector(7 downto 0);
19  signal count : integer := 0;
20  signal clk_music : std_logic;
21
22  -- Take the toneGenerator component
23  component toneGenerator is
24  port (toneOut : out std_logic; --this pin will give your notes output
25        clk : in std_logic;
26        LED : out std_logic_vector(7 downto 0);
27        switch : in std_logic_vector(7 downto 0));
28  end component toneGenerator;
29
30 begin
31
32  process(clk_50, clk_music, resetn) -- Fill sensitivity list
33  variable y_next_var : state_type;
34  variable n_count : integer := 0;
35  variable timecounter : integer range 0 to 1E8 := 0;
36  variable clk_c : std_logic := '1';
37
38  begin
39
40    y_next_var := y_present;
  
```

```

41      n_count := count;
42
43      --switch positions sa,re,ga,ma,pa,dha,ni,null
44      --led positions sa,re,ga,ma,pa,dha,ni
45
46      case y_present is
47
48          WHEN sa => --sa state
49              if (count = 29) then
50                  y_next_var := sa;
51              elsif (count = 30) then
52                  y_next_var := silent;
53              elsif (count = 24) then
54                  y_next_var := ni;
55              end if;
56              switch <= (0 => '1', others => '0');
57
58          WHEN re => --re state
59              if ((count = 23) or (count = 28)) then
60                  y_next_var := sa;
61              elsif (count = 27) then
62                  y_next_var := re;
63              elsif (count = 16) then
64                  y_next_var := ga;
65              end if;
66              switch <= (1 => '1', others => '0');
67
68          WHEN ga => --ga state
69              if ((count = 15) or (count = 22)) then
70                  y_next_var := re;
71              elsif ((count = 17) or (count = 18) or (count = 19)) then
72                  y_next_var := ga;
73              elsif ((count = 8) or (count = 20)) then
74                  y_next_var := ma;
75              end if;
76              switch <= (2 => '1', others => '0');
77
78          WHEN ma => --ma state
79              if ((count = 7) or (count = 14) or (count = 21)) then
80                  y_next_var := ga;
81              elsif ((count = 9) or (count = 10) or (count = 11)) then
82                  y_next_var := ma;
83              elsif (count = 12) then
84                  y_next_var := pa;
85              end if;
86              switch <= (3 => '1', others => '0');
87
88          WHEN pa => --pa state
89              if ((count = 6) or (count = 13)) then
90                  y_next_var := ma;
91              elsif ((count = 1) or (count = 2) or (count = 3)) then
92                  y_next_var := pa;
93              elsif (count = 4) then
94                  y_next_var := dha;
95              end if;
96              switch <= (4 => '1', others => '0');
97
98          WHEN dha => --pa state
99              if (count = 5) then
100                  y_next_var := pa;
101              end if;
102              switch <= (5 => '1', others => '0');
103
104          WHEN ni => --ni state
105              if (count = 26) then
106                  y_next_var := re;
107              elsif (count = 25) then
108                  y_next_var := ni;
109              end if;
110              switch <= (6 => '1', others => '0');
111
112          WHEN silent => --silent state
113              if (count = 31) then
114                  y_next_var := silent;
115              elsif ((count = 32) or (count = 0)) then
116                  y_next_var := pa;
117              end if;
118              switch <= (7 => '1', others => '0');
119
120          WHEN others =>


```

```

121     y_next_var := Silent;
122     switch <= (7 => '1', others => '0');
123
124     END CASE ;
125
126     -- generate 4Hz clock (0.25s time period) from 50MHz clock (clock_music)
127     if (clk_50 = '1' and clk_50' event) then
128         if timecounter = 6250000 then -- The cycles in which clk is 1 or 0
129             timecounter := 1; -- When it reaches max count i.e. 25x10^6 (half a second) it will be 0 again
130             clk_c := not clk_c; -- this variable will toggle
131         else
132             timecounter := timecounter + 1; -- Counter will be incremented till it reaches max count
133         end if;
134     end if;
135     clk_music <= clk_c;
136
137     -- state transition
138     if (clk_music = '1' and clk_music' event) then
139         if (resetrn = '1') then
140             y_present <= Silent;
141             count <= 0;
142         else
143             y_present <= y_next_var;
144             if (count = 32) then
145                 count <= 0;
146             else
147                 count <= count + 1;
148             end if;
149         end if;
150     end if;
151 end process;
152
153 -- instantiate the component of toneGenerator
154 tone_gen: toneGenerator port map (toneOut, clk_50, LED, switch);
155 end fsm;

```


State Machine Viewer:

 

DUT Input/Output Format:

Not needed for this experiment.

RTL Simulation:

 

Gate-level Simulation:

Not needed for this experiment.

Krypton board:

Screenshot of Pin Planning:

Node Name	Direction	Location	I/O Bank	Header Location	I/O Standard	Reserved	Current Strength	Differential Pair	IO Preservation
in clk_50	Input	PIN_89	3	PIN_89	3.3-...VTTL		16mA...ult)		
out LED[7]	Output	PIN_49	4	PIN_49	3.3-...VTTL		16mA...ult)		
out LED[6]	Output	PIN_50	4	PIN_50	3.3-...VTTL		16mA...ult)		
out LED[5]	Output	PIN_51	4	PIN_51	3.3-...VTTL		16mA...ult)		
out LED[4]	Output	PIN_52	4	PIN_52	3.3-...VTTL		16mA...ult)		
out LED[3]	Output	PIN_53	4	PIN_53	3.3-...VTTL		16mA...ult)		
out LED[2]	Output	PIN_55	4	PIN_55	3.3-...VTTL		16mA...ult)		
out LED[1]	Output	PIN_57	4	PIN_57	3.3-...VTTL		16mA...ult)		
out LED[0]	Output	PIN_58	4	PIN_58	3.3-...VTTL		16mA...ult)		
in resetn	Input	PIN_48	4	PIN_48	3.3-...VTTL		16mA...ult)		
out toneOut	Output	PIN_1	1	PIN_1	3.3-...VTTL		16mA...ult)		

Observations:

The RTL simulation gave a correct result. After mapping the circuit to the Krypton Board, the music played was also as expected, demonstrating the correctness of the design.

References:

Lectures and Tutorials by the EE 214 team Lectures by Prof. M.P. Desai
